

Module 5

Two-Port Networks and Network Graphs


To

Dr. Elizabeth Rufus


Professor, School of Electronics Engineering

Tutorial

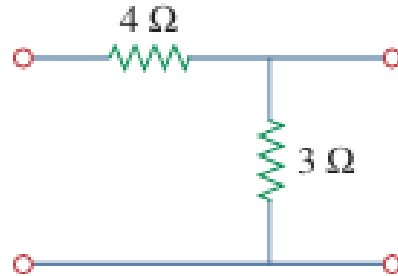
1. Find the z parameters of the two-port network in the figure below.



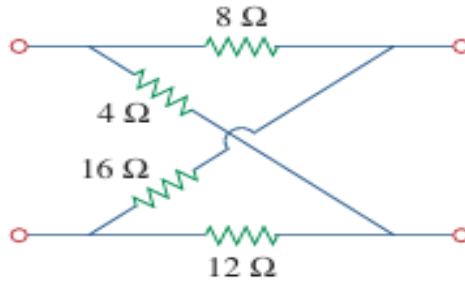2. Determine the z parameters for the circuit.




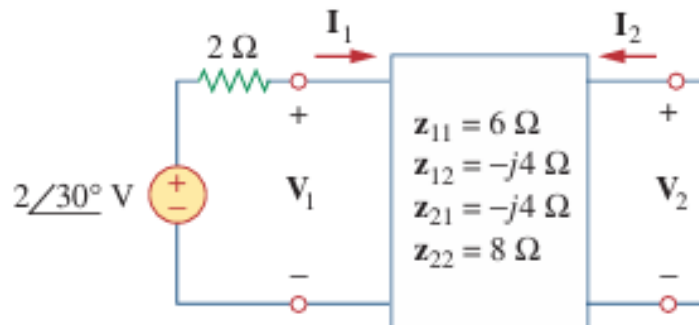3. Calculate and in the two-port of the circuit shown below.




Tutorial

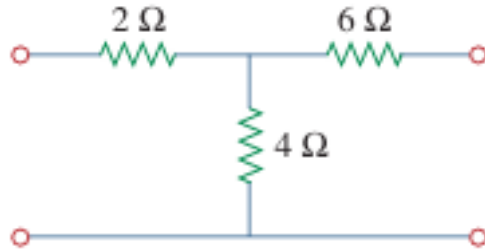
4. Obtain the y parameters for the T network shown in the figure below.



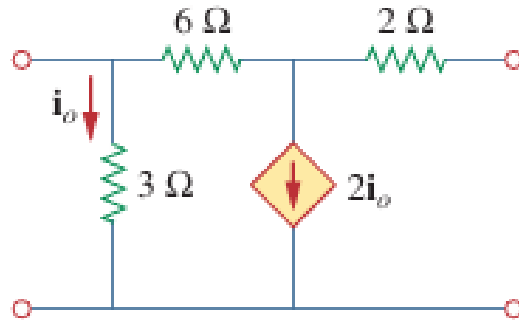5. Obtain the y parameters for the circuit.




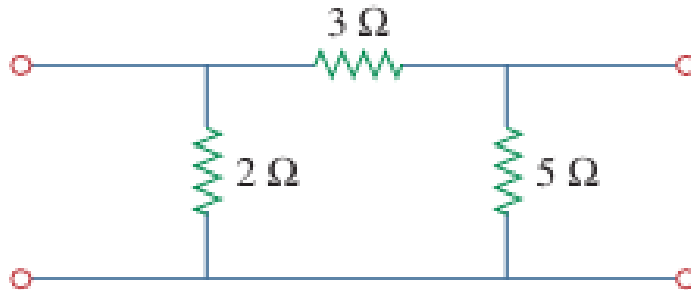6. Determine the h parameters for the circuit.




Tutorial

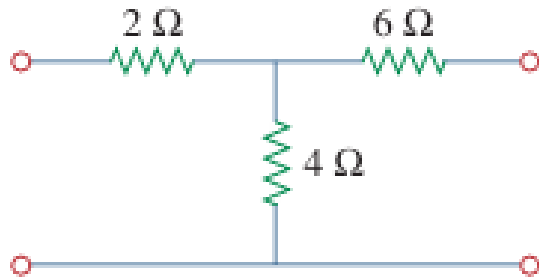7. Find the transmission parameters for the circuit.



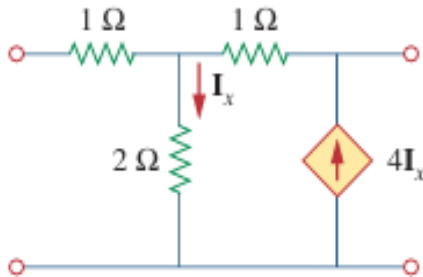8. Find the transmission parameters for the circuit



9. Obtain the transmission parameters for the network

