

Module 3


Sinusoidal Steady-State Analysis

Dr. Elizabeth Rufus


Professor, School of Electronics Engineering

Tutorial

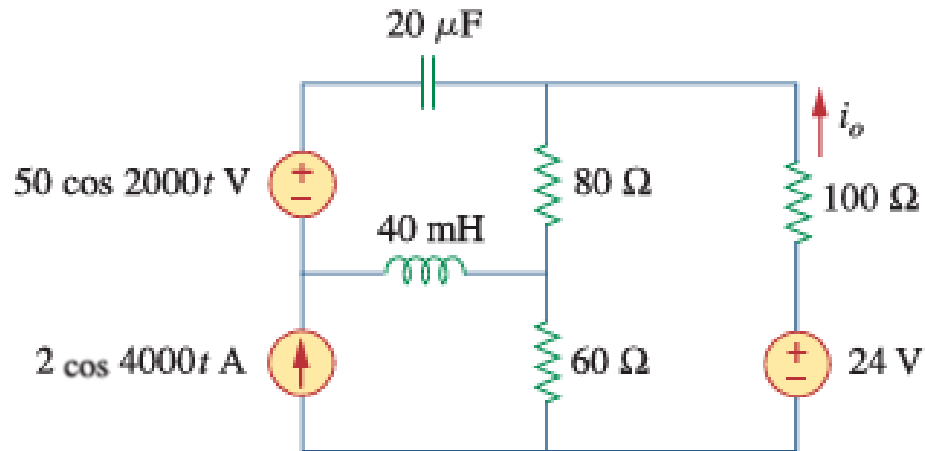1. Find i_o in the circuit using Superposition theorem.



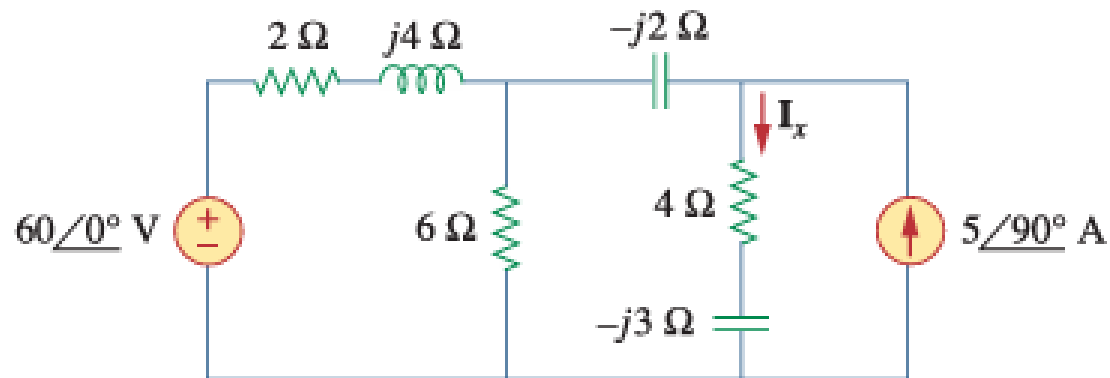2. Find I_x in the circuit using the concept of Source transformation.



Tutorial

3. Find V_0 in the circuit using Source transformation.

