

Module 3


Sinusoidal Steady-State Analysis

Dr. Elizabeth Rufus


Professor, School of Electronics Engineering

Tutorial

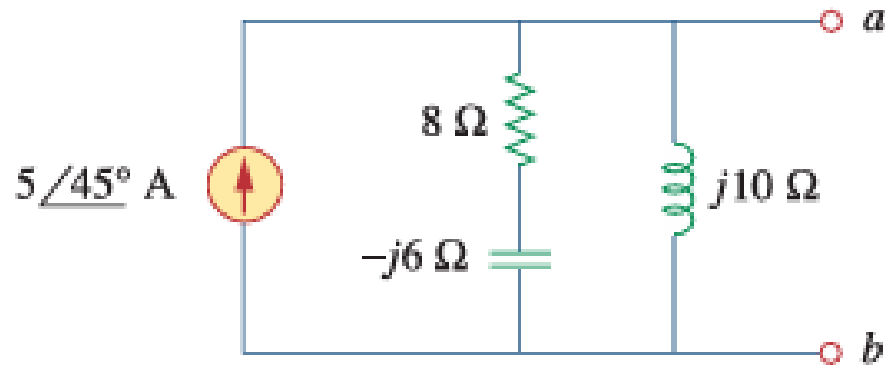1. For the circuit in the figure, find the Thevenin equivalent at the terminals a-b.




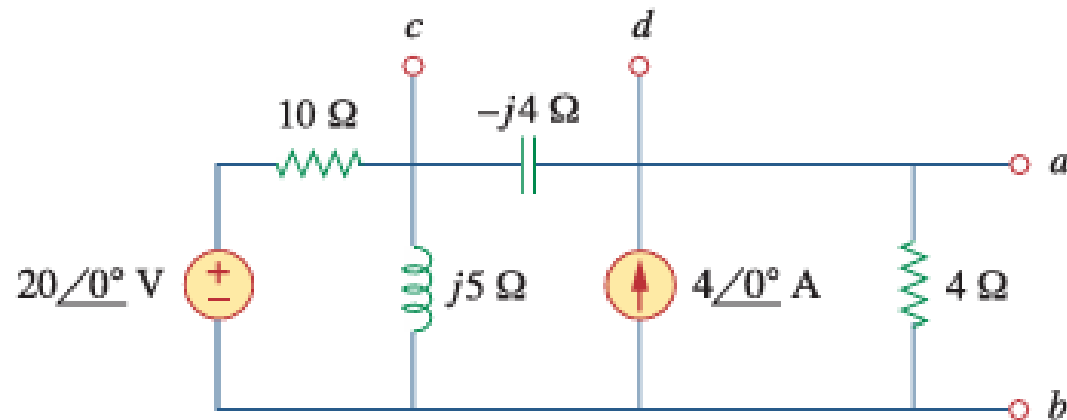2. Find Thevenin equivalent of the circuit as seen from : (a) terminals a-b ,(b) terminals c-d.




Tutorial

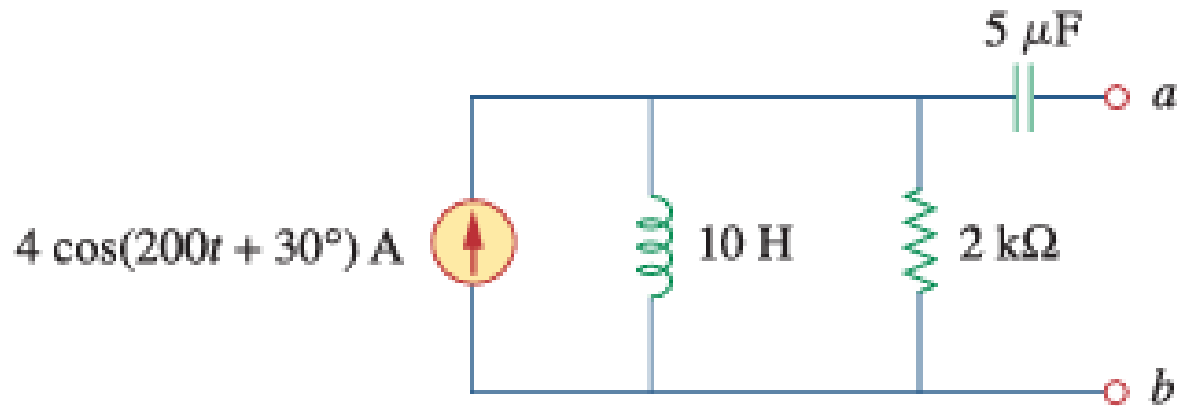3. Determine the Norton equivalent of the circuit at terminals a-b.



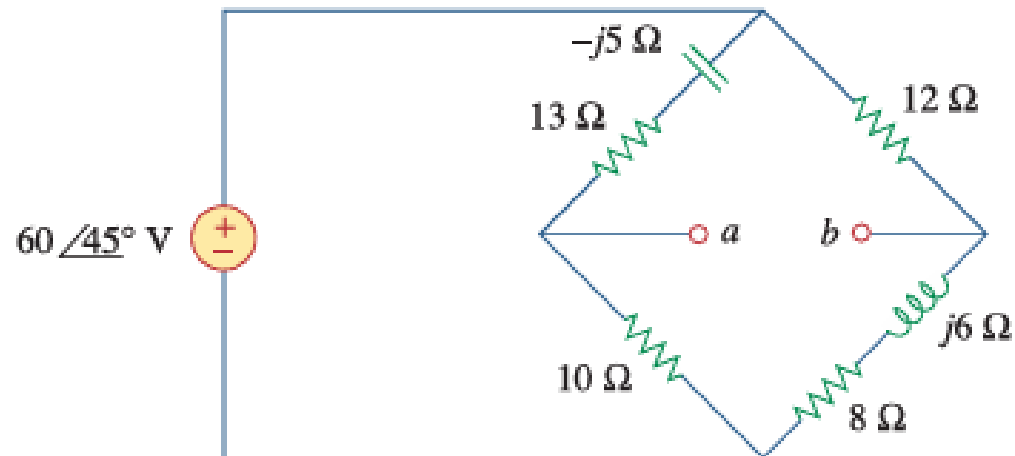4. Determine the Norton equivalent of the circuit at terminals a-b.



Tutorial

5. Determine the maximum average power delivered to the load for the circuit.

